



Semiconductor Memory Organization & Addressing

Organización del Computador 2025

Basel - Ferreyra - Laprovitta - Vélez - Vodanovic

FAMAF

Facultad de Matemática,
Astronomía, Física y
Computación




UNC

Universidad
Nacional
de Córdoba

Introduction

- ❑ Computer systems functionality aspects
 - Processing
 - Transformation of data
 - Implemented using processors
 - Storage
 - Retention of data
 - Implemented using memory
 - Communication
 - Transfer of data between processors and memories
 - Implemented using buses
 - Called *interfacing*

A simple bus

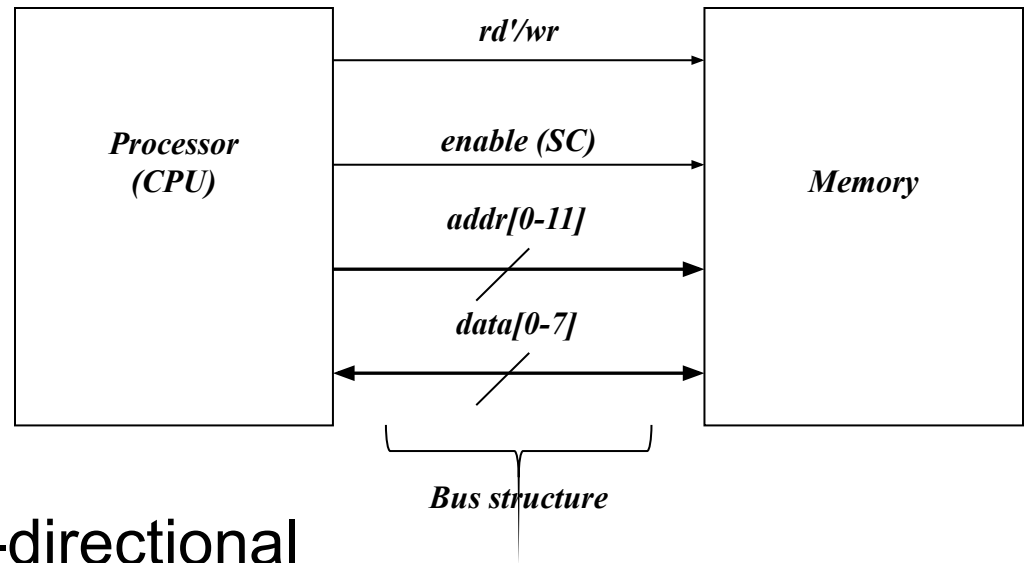

□ Wires:

- Uni-directional or bi-directional
- One line may represent multiple wires


□ Bus

- Set of wires with a single function
 - Address bus, data bus
- Or, entire collection of wires
 - Address, data and control
 - Associated protocol: rules for communication


Semiconductor Memory Classification

Read-Write Memory		Non-Volatile Read-Write Memory	Read-Only Memory
Random Access	Non-Random Access	EPROM EEPROM FLASH	Mask-Programmed Programmable (PROM)
SRAM DRAM	FIFO LIFO Shift Register CACHE		

Memory Timing: Definitions

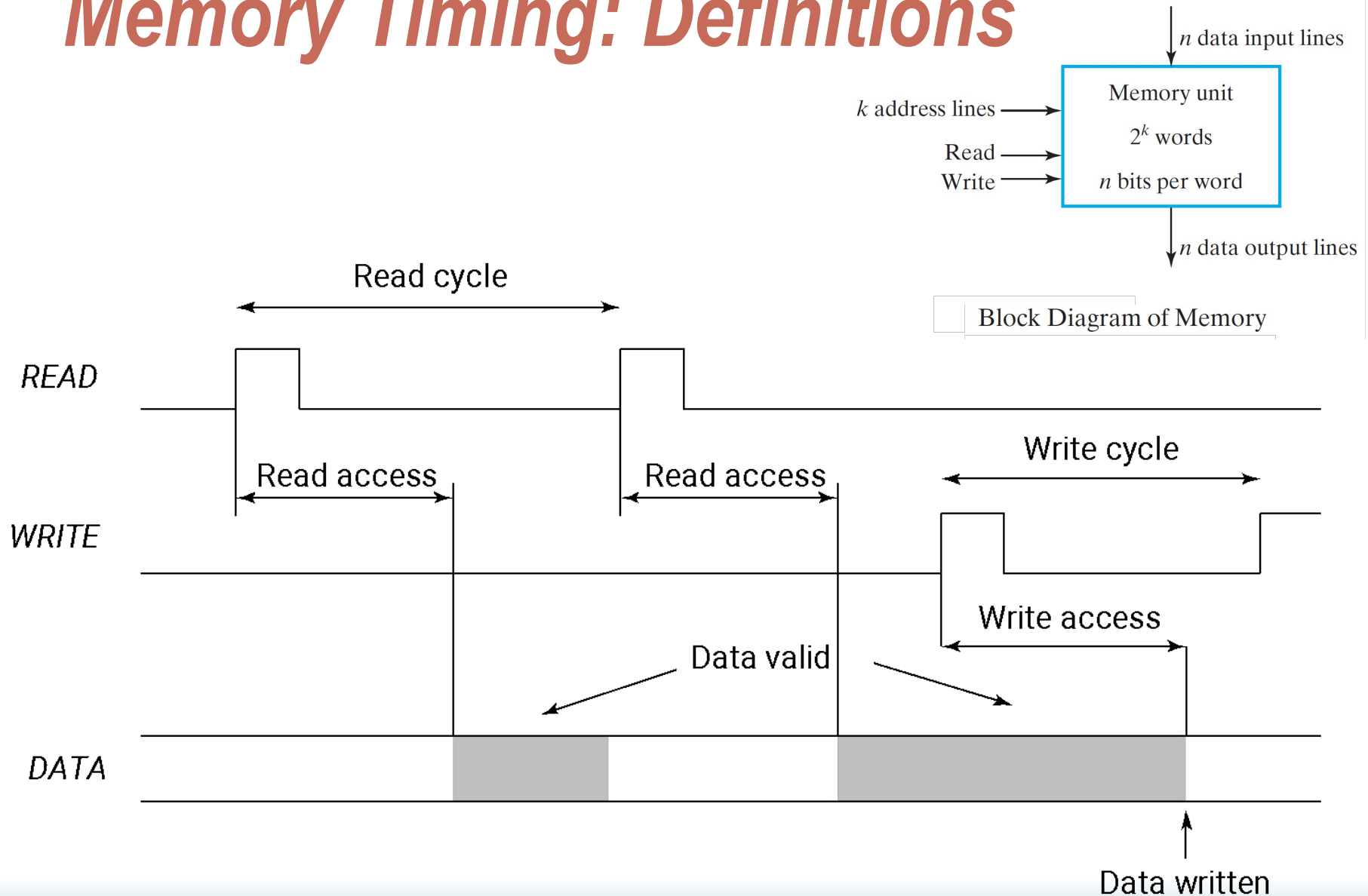

Control Inputs to a Memory Chip

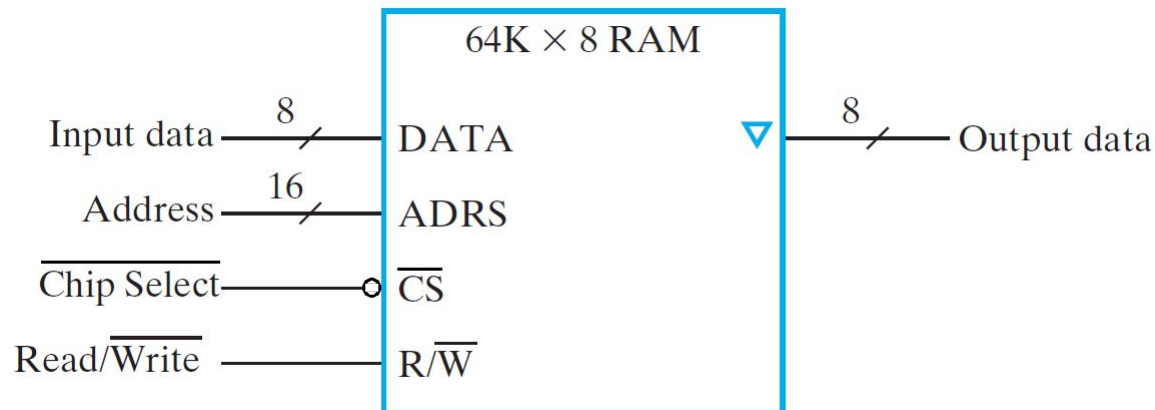

Chip Select \overline{CS}	Read/Write R/\overline{W}	Memory Operation
1	×	None
0	0	Write to selected word
0	1	Read from selected word


Memory Organization

Memory Address		Word (8 bits)							
Binary	Dec								
0000000000	0	0	1	1	1	0	0	1	0
0000000001	1	1	1	1	1	1	1	1	1
0000000010	2	0	0	0	1	0	0	1	1
.
.
1111111101	1021	1	1	1	1	0	0	0	1
1111111110	1022	1	1	0	0	0	0	0	0
1111111111	1023	0	0	0	0	1	1	1	1


Addressed word

Storage bit cell

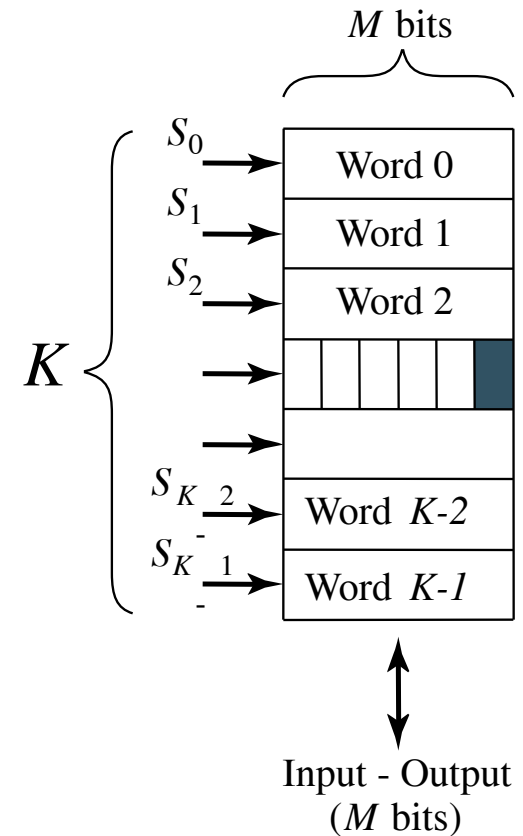**Example organization for
1Kword x 8 bits = 8K bits memory**




Memory Architecture: Decoders

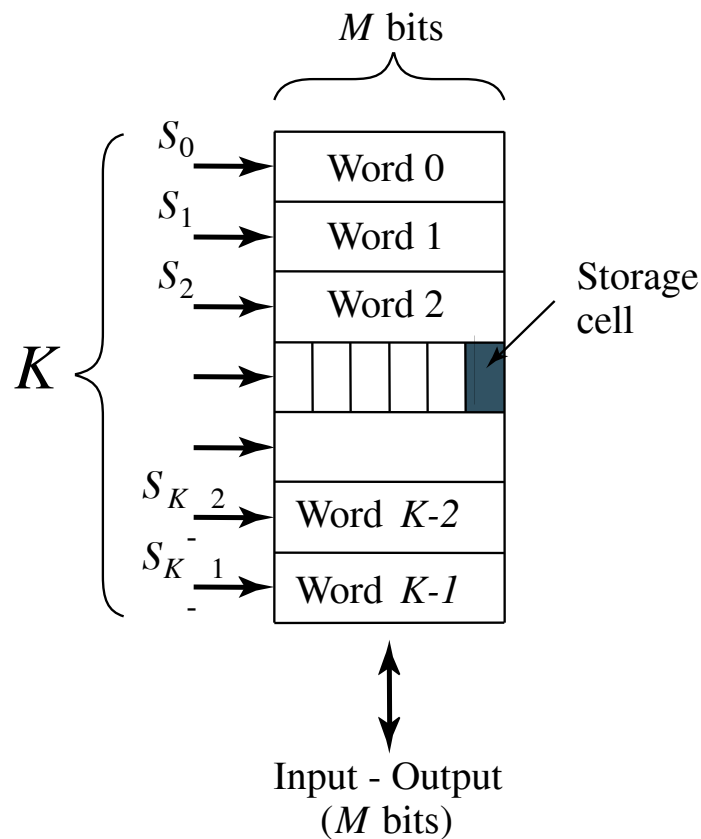

Intuitive architecture for $K \times M$ memory


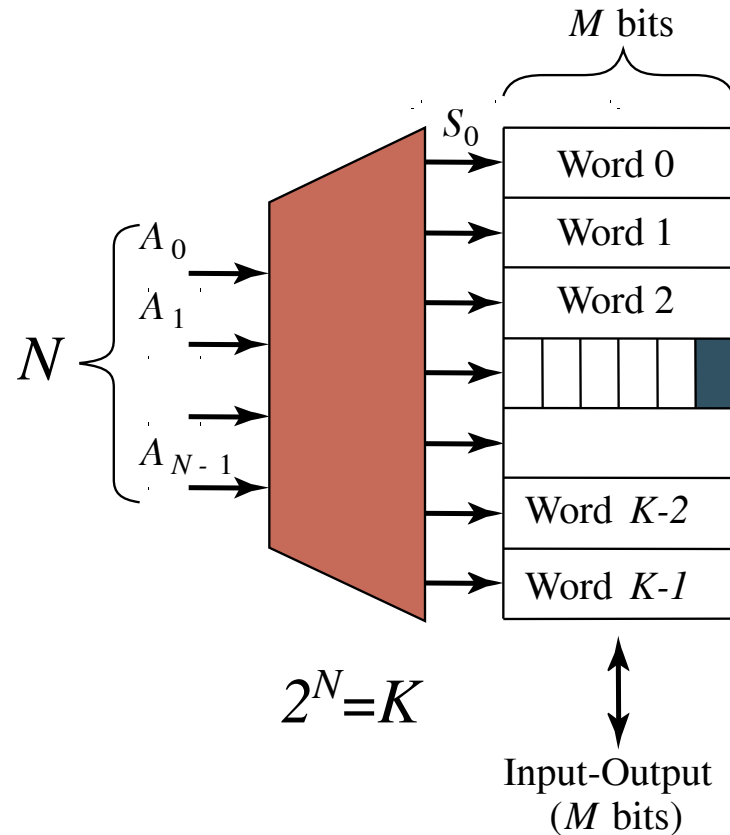
Too many select signals:
 K words == K select signals



Decoder reduces the number of select signals
 $N = \log_2 K$


Array-Structured Memory Architecture

Problem: ASPECT RATIO or HEIGHT >> WIDTH

 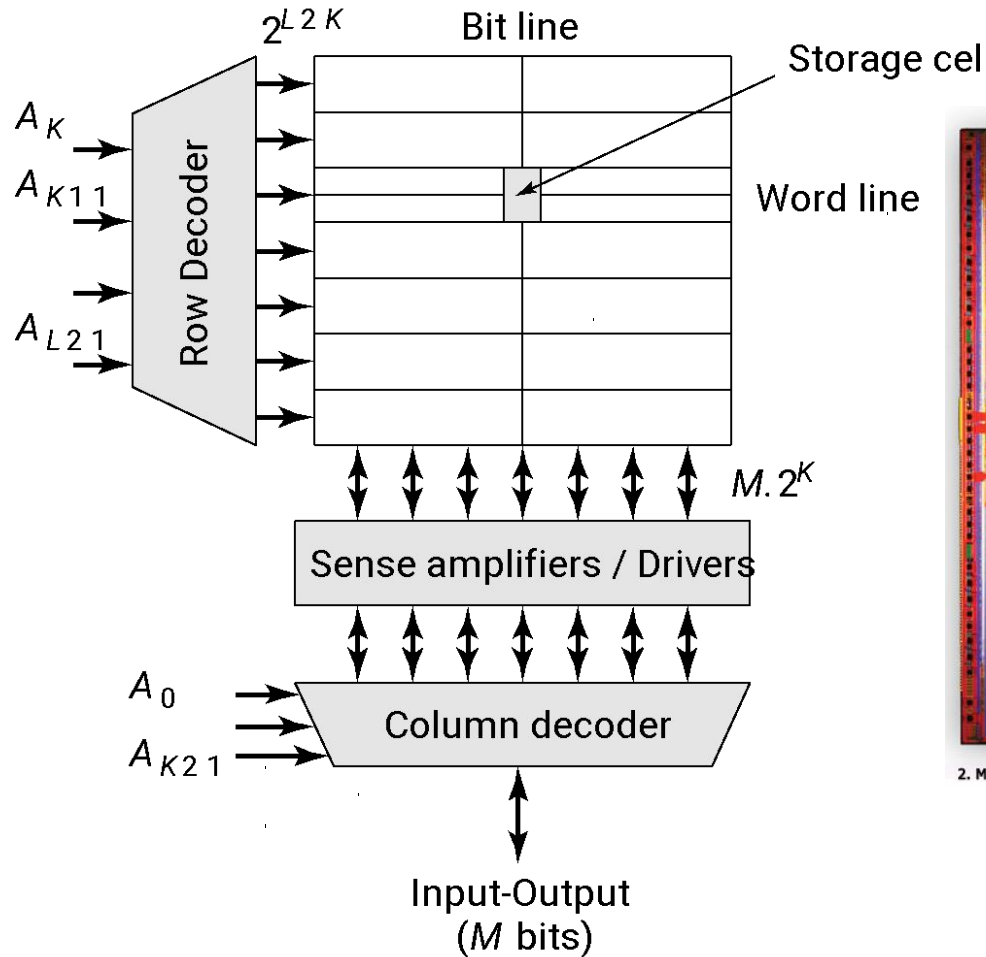

2. Micron's triple-level cell (TLC) flash memory stores 3 bits of data in each transistor.

Hierarchical Memory Architecture

 


Advantages

1. Shorter wires within

Block address activates only 1 block => power savings

Addressable Space

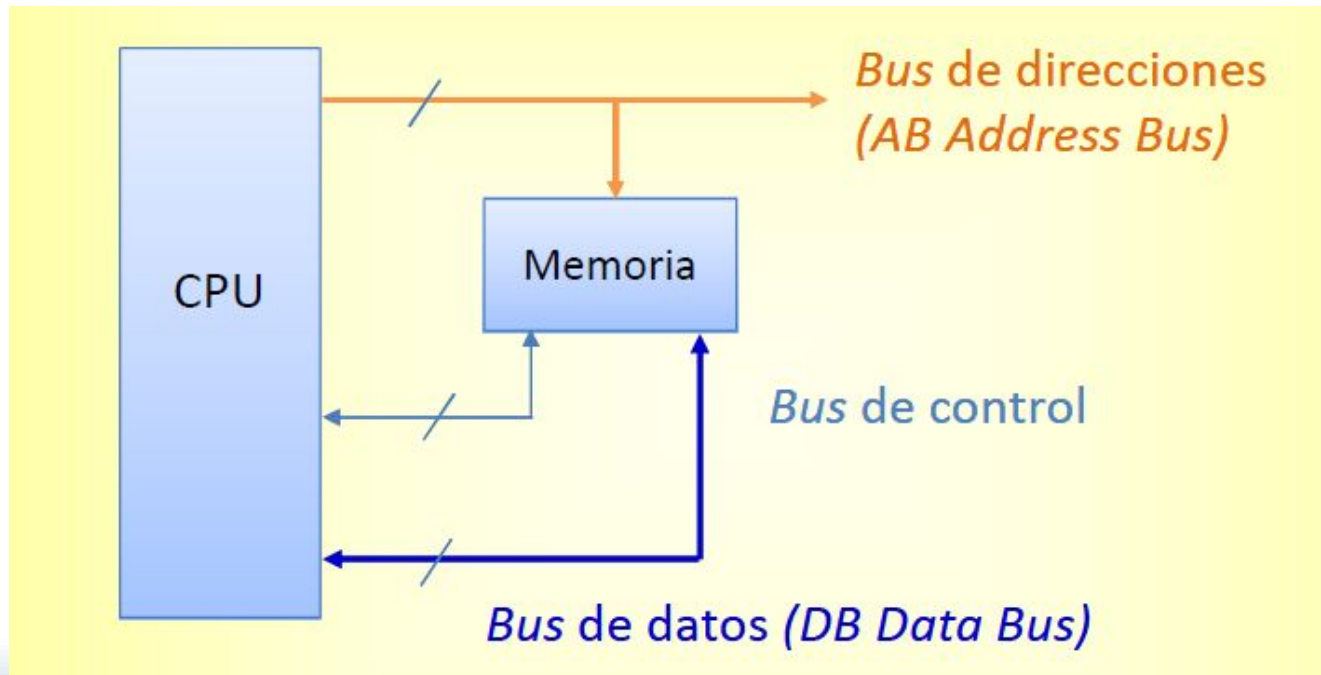- ❑ It's defined as the **total number** of addresses the CPU can access.
- ❑ It depends on the width (number of bits) of the address bits: **n bits $\rightarrow 2^n$ addresses**




Size prefixes and symbols

N bits (2^N)	Capacidad (en words)
2^1 =	2 words
2^2 =	4 words
2^3 =	8 words
2^4 =	16 words
2^5 =	32 words
2^6 =	64 words
2^7 =	128 words
2^8 =	256 words
2^9 =	512 words


N bits (2^N)	Capacidad (en words)	Simbolo [Prefijo]
2^{10} =	1024 words	= 1Kw [Kilo]
2^{20} =	1024 Kw	= 1Mw [Mega]
2^{30} =	1024 Mw	= 1Gw [Giga]
2^{40} =	1024 Gw	= 1Tw [Tera]
2^{50} =	1024 Tw	= 1Pw [Peta]

SIZE	PREFIX	SYMBOL	SIZE	PREFIX	SYMBOL
10^3	Kilo-	K	2^{10}	Kibi-	Ki
10^6	Mega-	M	2^{20}	Mebi-	Mi
10^9	Giga-	G	2^{30}	Gibi-	Gi
10^{12}	Tera-	T	2^{40}	Tebi-	Ti
10^{15}	Peta-	P	2^{50}	Pebi-	Pi
10^{18}	Exa-	E	2^{60}	Exbi-	Ei
10^{21}	Zetta-	Z	2^{70}	Zebi-	Zi
10^{24}	Yotta-	Y	2^{80}	Yobi-	Yi
10^{-3}	milli-	m	10^{-15}	femto-	f
10^{-6}	micro-	μ	10^{-18}	atto-	a
10^{-9}	nano-	n	10^{-21}	zepto-	z
10^{-12}	pico-	p	10^{-24}	yocto-	y

Memory Addressing (data bus)

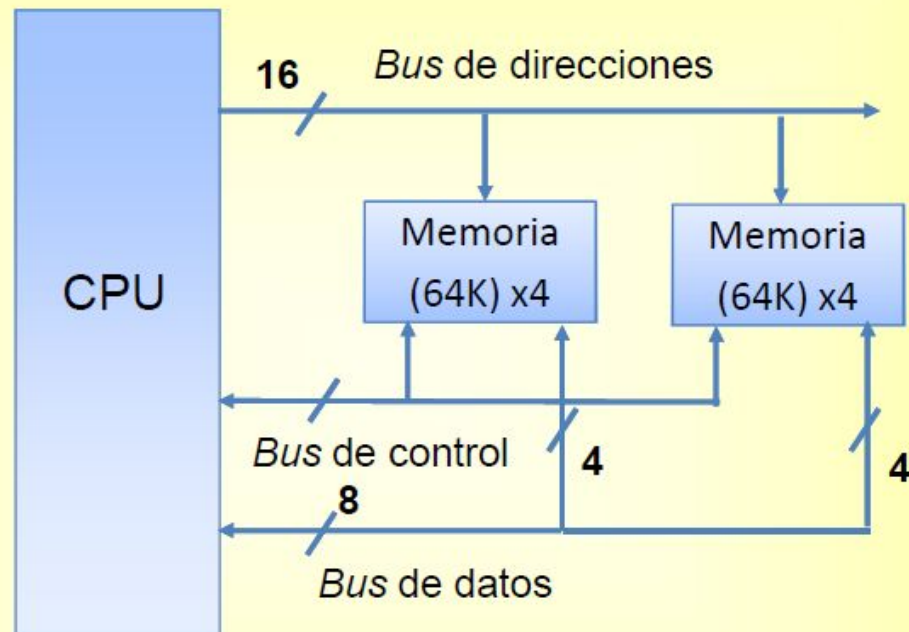


Memory Addressing (address bus)

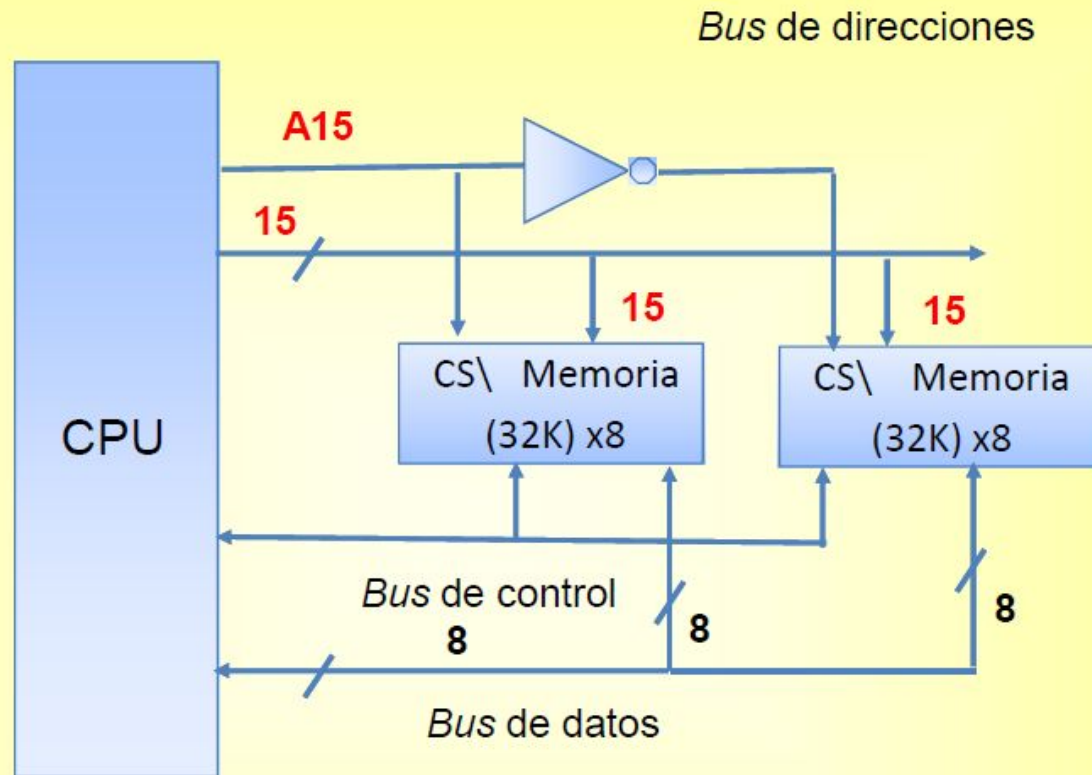

Memory Addressing (parallel)

A ₉ . . . A ₀	D ₁₅ . . . D ₈	D ₇ . . . D ₀
0000000000	0 1 . 1	0 . 1 0
0000000001	1 1 . 1	1 . 1 1
0000000010	0 0 . 1	0 . 1 1

1111111101	1 1 . 1	0 . 0 1
1111111110	1 1 . 0	0 . 0 0
1111111111	0 0 . 0	1 . 1 1

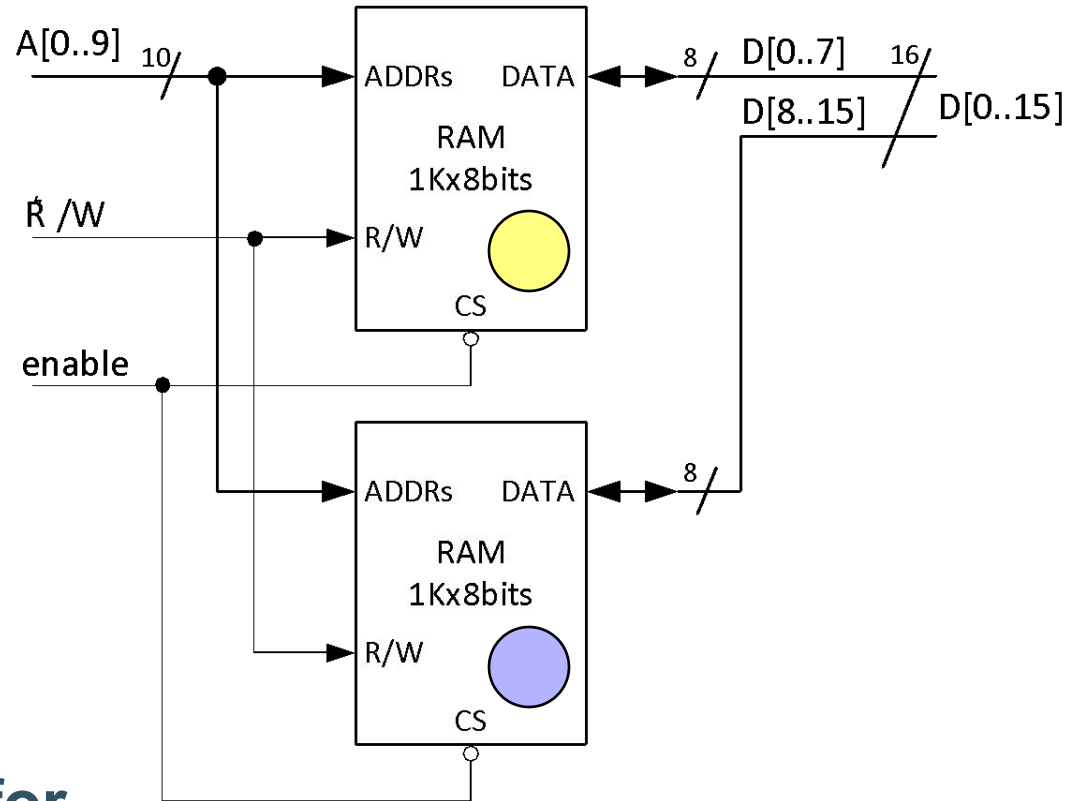



**Example organization for
bank of 1Kword x 16 bits
from 2 x 1Kx8bits**

Memory Addressing (serial)


A ₁₁	A ₁₀	A ₉	. . .	A ₀	D ₇	. . .	D ₀					
0	0	0000000000			0	1	1	1	0	0	1	0
				
0	0	1111111111			0	0	0	1	0	1	1	1
0	1	0000000000			0	1	1	1	0	0	1	0
				
0	1	1111111111			0	0	0	1	0	1	1	1
1	0	0000000000			0	1	1	1	0	0	1	0
				
1	0	1111111111			0	0	0	1	0	1	1	1
1	1	0000000000			0	1	1	1	0	0	1	0
				
1	1	1111111111			0	0	0	1	0	1	1	1

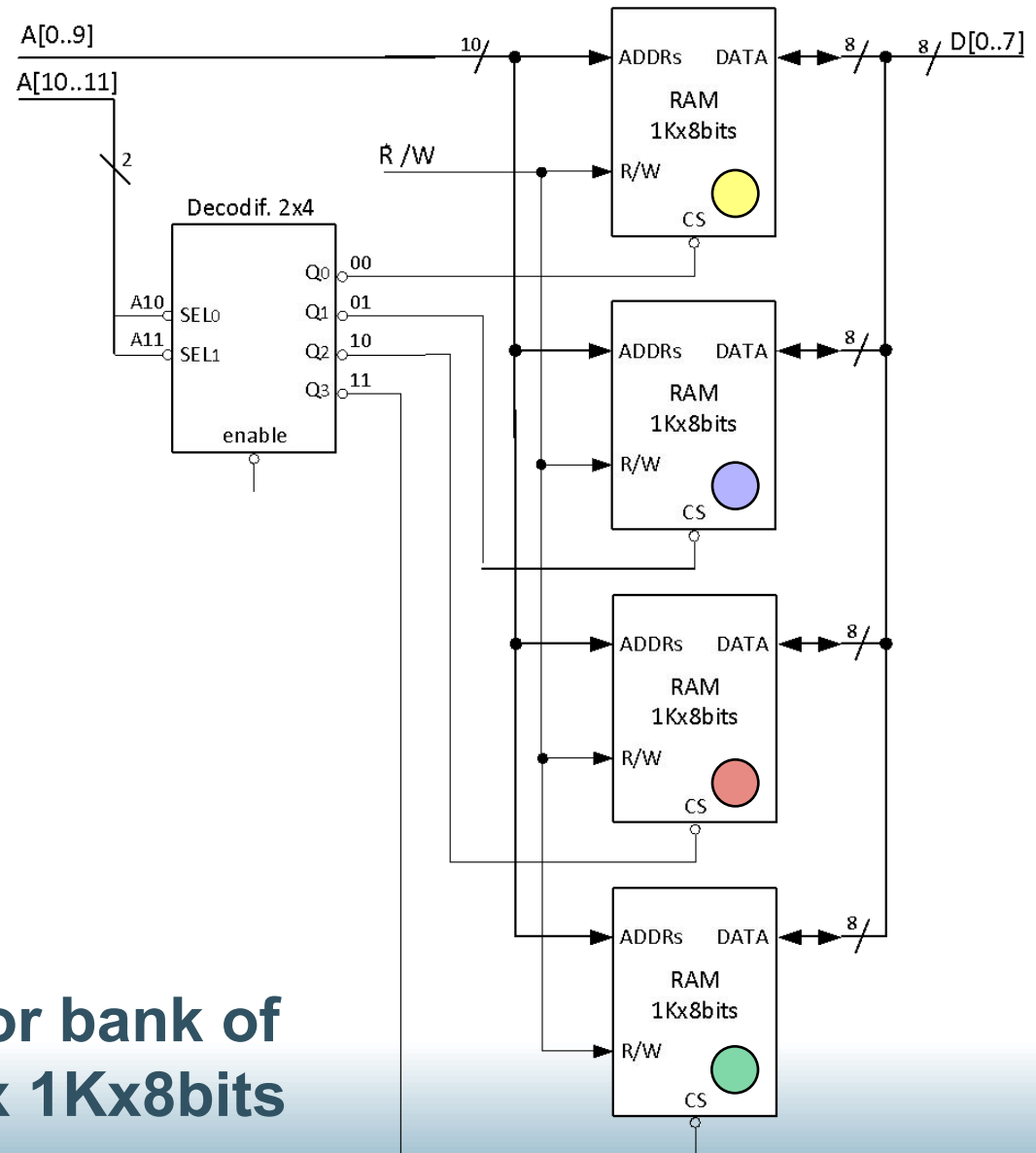Example organization for bank of 4Kword x 8 bits from 4 x 1Kx8bits



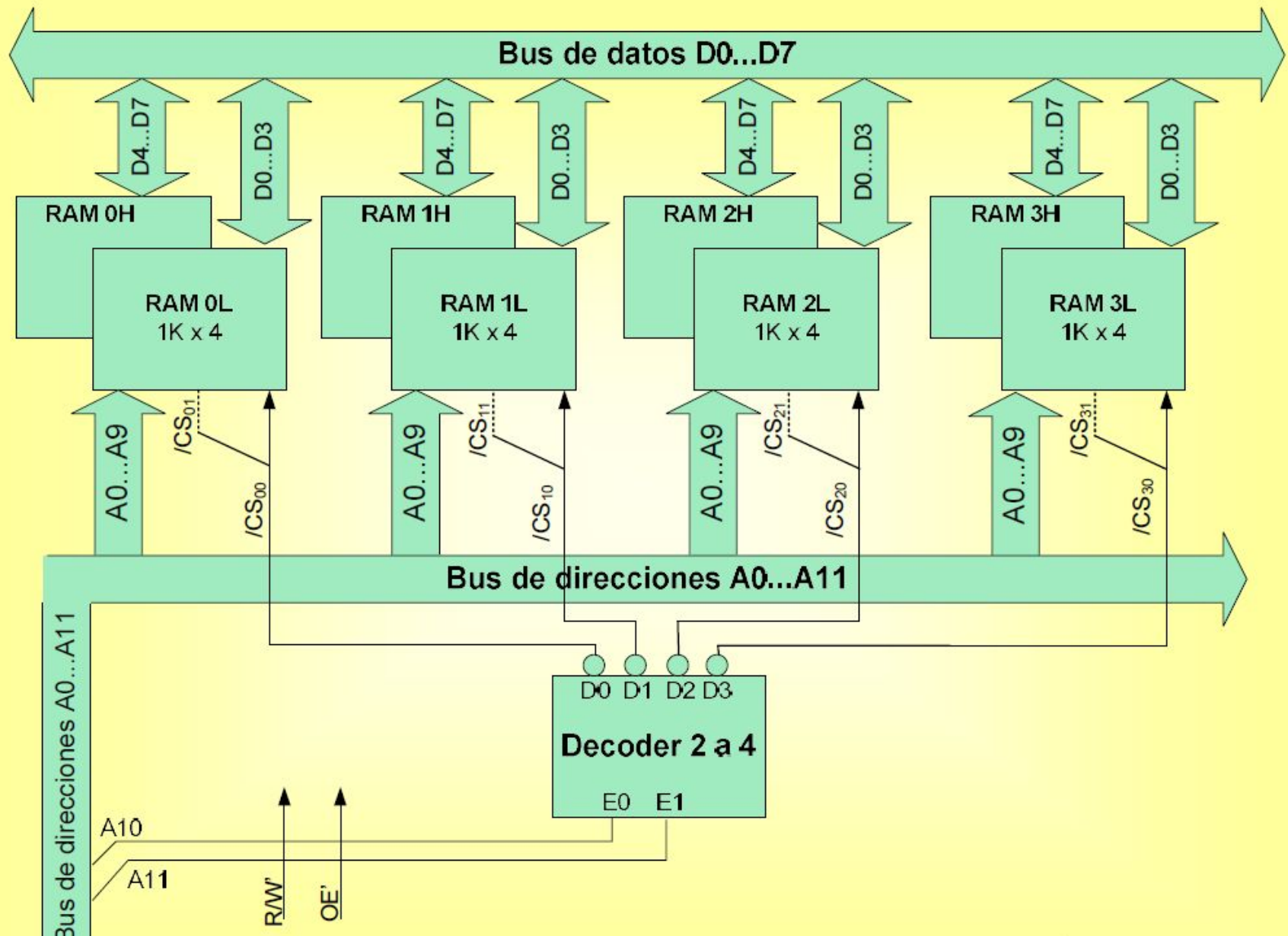


Example: Conventional PC Memory map

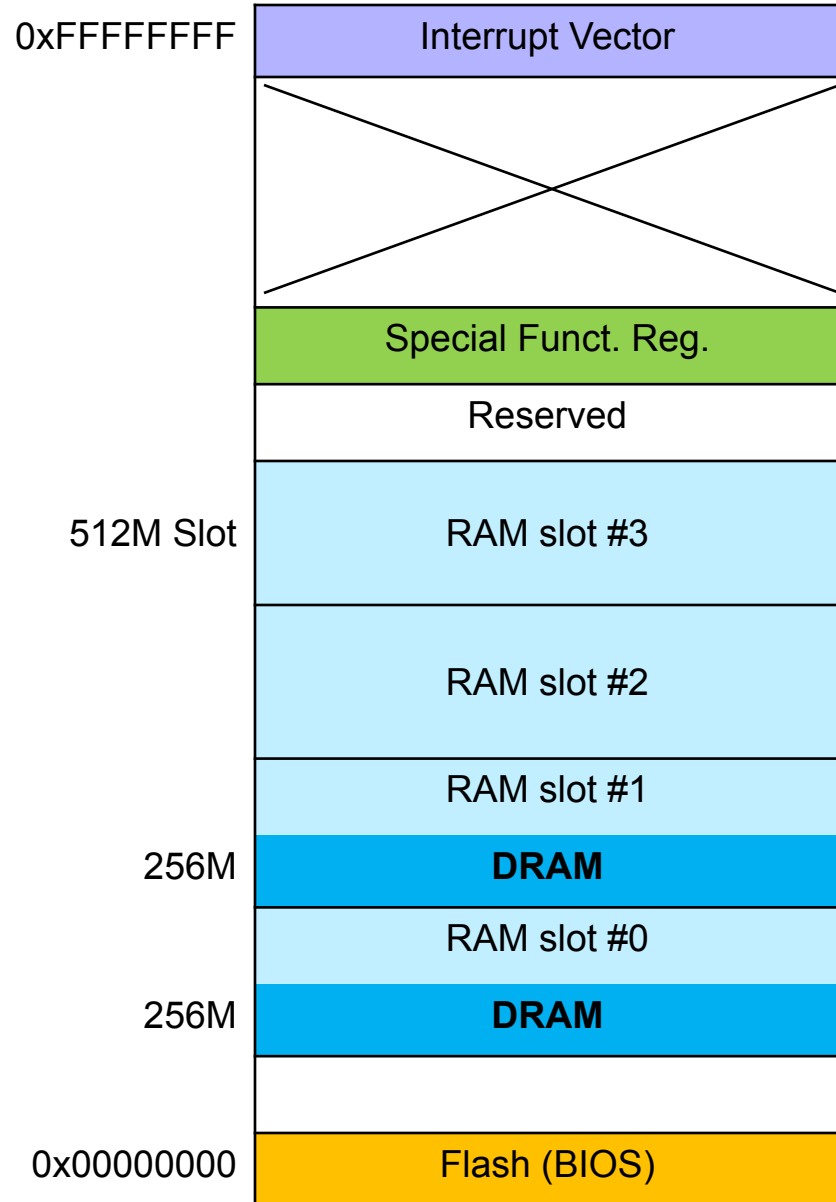

‘Espejos’ en el mapa de memoria

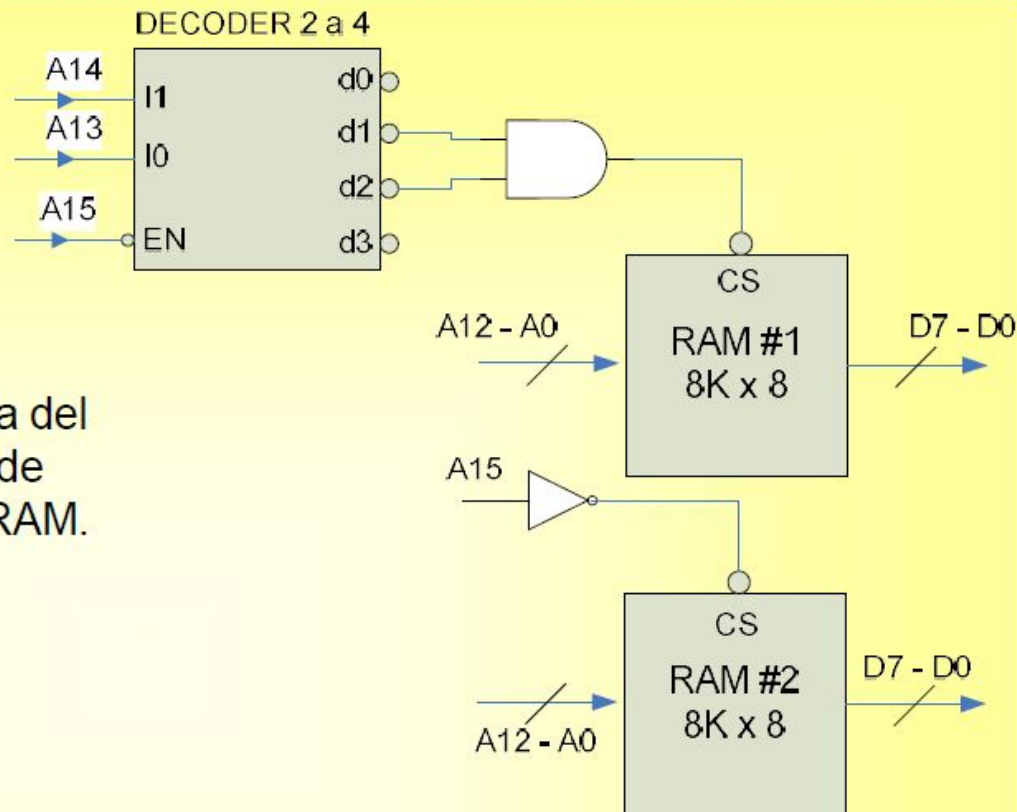Caso: Hallar el mapa de memoria del circuito indicando las posiciones de memoria ocupadas por cada CI RAM.



A15	A14	A13	Decoder	Mem	Posición en el mapa	Bytes
0	0	0	d0	-	H0000 – H1FFF	8K
	0	1	d1	RAM1	H2000 – H3FFF	8K
	1	0	d2	RAM1	H4000 – H5FFF	8K
	1	1	d3	-	H6000 – H7FFF	8K
1	X	X		RAM2	H8000 - HFFFF	32K

Bibliografía: M. Morris Mano, Charles R. Kime, and Tom Martin, "Logic and computer design fundamentals" 5th Edition (2015).